

2001 IMPALA/MONTE CARLO PARKING LIGHT ISOLATION

Following the below wiring diagram will prevent the activation of the SERVICE ENGINE SOON light during remote start.

Diagram A


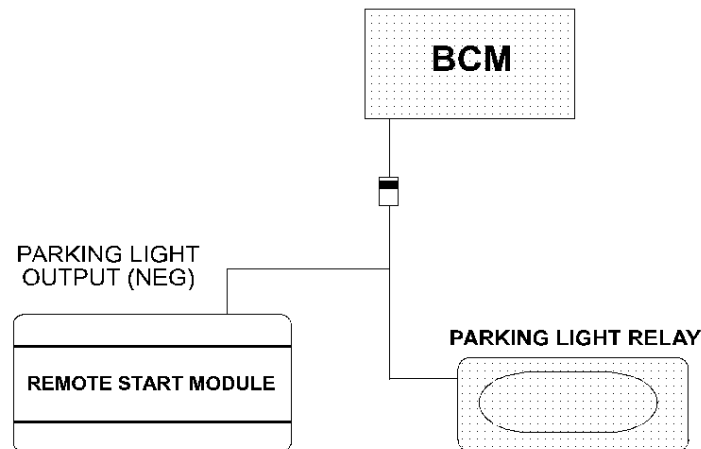


Diagram B

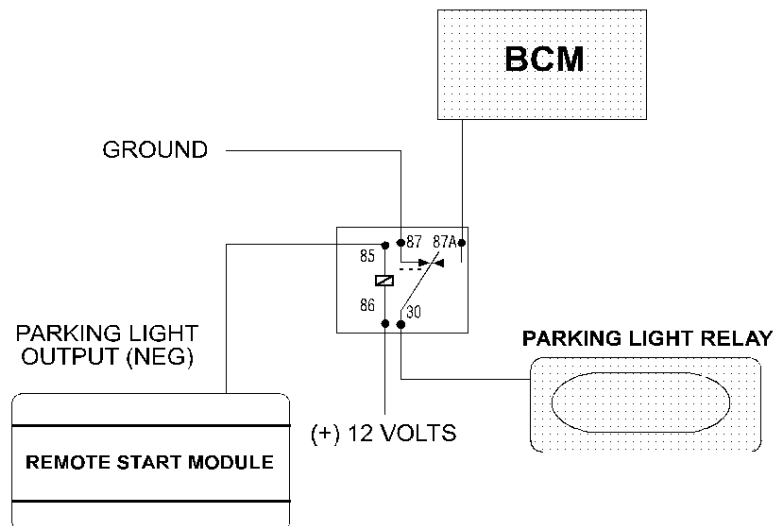

IMPORTANT! This wiring information is being provided free of charge on an "as is" basis, without any representation or warranty. It is the dealer's responsibility to verify any circuit before interfacing with it using a digital multi-meter. Directed Electronics Inc. assumes no responsibility with regards to the accuracy or currency of this information. Proper installation in every case remains the responsibility of the installer.