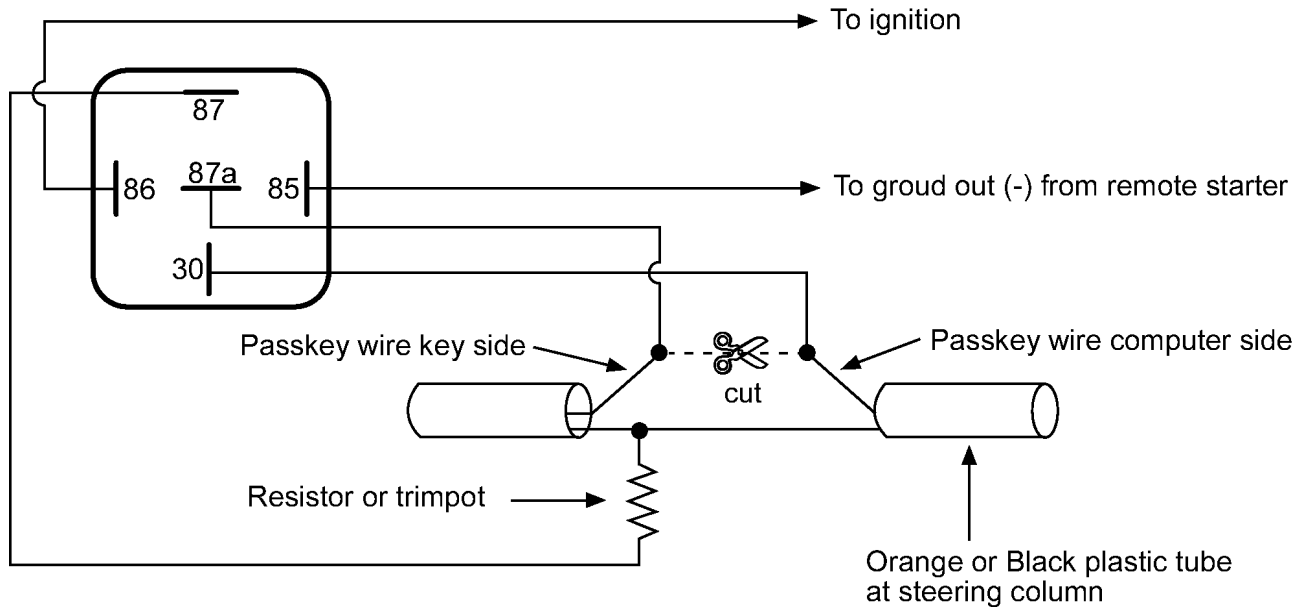


PASSKEY / VATS anti-theft bypass



This system uses a resistor in the key, use a digital volt meter set to ohms and put 1 lead on each side of the vats chip in the center of the key, find a resistor to match your reading and proceed to wire a relay as per the diagram. Locate the Orange or black tube running down the steering column from the ignition switch. Cut open the tube to expose the passkey wires inside. Your resistor or trumpet should be within +/- 10 ohms of the key. Either of the passkey wires can be cut. GM uses only a fixed number of different resistors with their **PASSKEY/VATS** system, your measurement should correspond to one of the following values.

390 Ohms	1800 Ohms	7500 Ohms
520 Ohms	2370 Ohms	9530 Ohms
680 Ohms	3010 Ohms	11800 Ohms
885 Ohms	3740 Ohms	
1130 Ohms	4750 Ohms	
1470 Ohms	6040 Ohms	

NOTE: The information on this sheet is provided on an "as is" basis with no representation or warranty of accuracy whatsoever. It is the sole responsibility of the installer to check and verify any circuit before connecting to it. Only a computer safe logic probe or digital multimeter should be used. Wiremagic.com Corp. assumes absolutely no liability or responsibility whatsoever pertaining to the accuracy or currency of the information supplied. The installation in every case is the sole responsibility of the installer performing the work and Wiremagic.com Corp. assumes no liability or responsibility whatsoever resulting from any type of installation, whether performed properly, improperly or any other way. The information supplied is a guide only.